
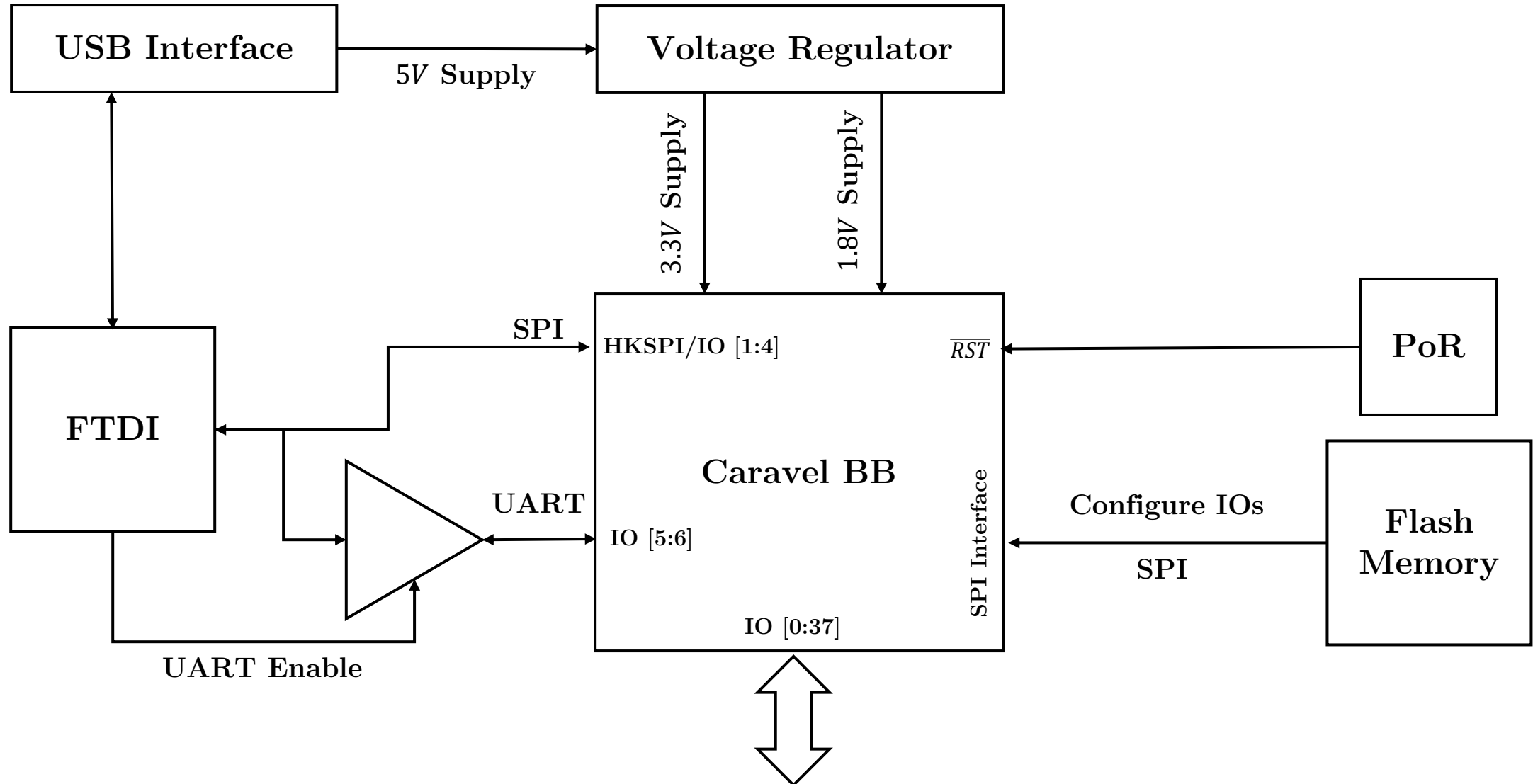


Caravel + Nucleo Board

Caravel Board V4 Block Diagram

 

Nucleo Board: ST Morpho Connectors




[1]: <https://os.mbed.com/platforms/ST-Nucleo-F429ZI/#board-pinout>

Nucleo Board: Interface with Caravel

- *CN4* jumpers in ST-Link part is used to program ST32 microcontroller, hence, configuring Caravel I/Os
- The board has a 3.3V Regulator (Max 500mA)
- Default clock supply is 8 MHz from ST-Link on *PF0*
- Caravel SPI/HKSPI interface could be on *PE11:PE14* or *PF6:PF9*
- Caravel UART interface could be on *PC10:PC11*
- *PA13* and *PA14* are shared with SWD signals connected to ST-LINK. If ST-LINK part is not cut, it is not recommended to use them as I/Os.
- Caravel BB dimensions would be 67.5mm × 92.5mm

Caravel + Nucleo Board Block Diagram

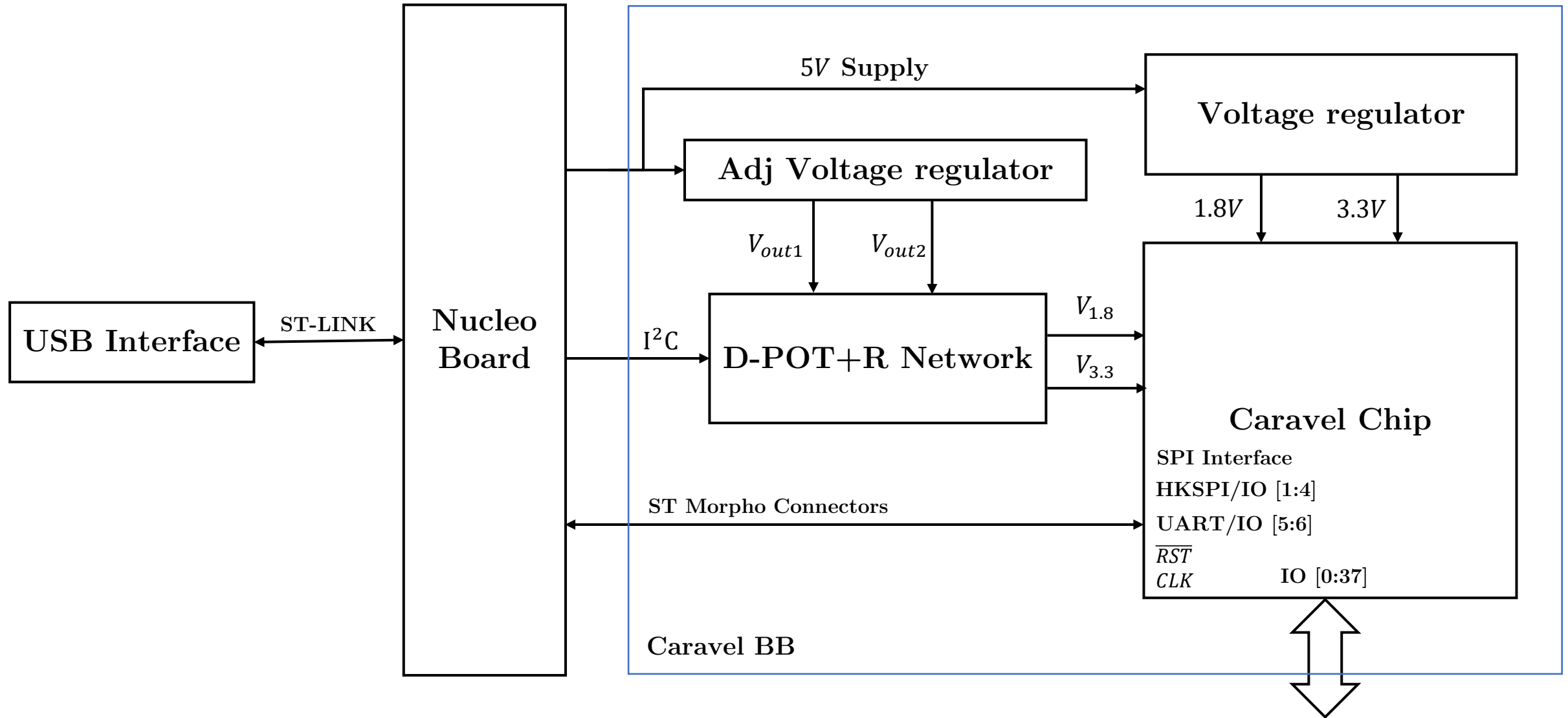

Dynamic Voltage Scaling (DVS)

- Dynamic power supply is required to test the chip with non-nominal supplies
- The required ranges are from 1.4V to 2.2V for $V_{1.8}$ and 3V to 3.6V for $V_{3.3}$
- Adjustable dual LDO (MIC2211) is capable of supplying from 1.25V to 5V at 150mA for V_{out1} and at 300mA for V_{out2}
- A digital potentiometer (D-POT) could be used with R network to dynamically tune the voltage outputs of the LDO using I^2C on $PF0:PF1$
- D-POT (10 k Ω device) range to be used in the calculations is from 0 k Ω to 7 k Ω , since its maximum resistance range is from 8 k Ω to 12 k Ω
- MCP4661 has 257 taps

$$N = \frac{R_{MAX}}{R_{TOT}} * 256 = 179.2 \approx 179$$
$$R_{step} = \frac{R_{TOT}}{256} = 39 \Omega$$

Resistance Calculations

- For $V_{1.8}$,

$$\begin{aligned} V_{out1min} &= 1.4V & V_{out1max} &= 2.2V \\ R_{LSmax} &= 3\text{ k}\Omega & V_{Ref} &= 1.25V \end{aligned}$$

$$V_{out1min} = V_{Ref} \left(1 + \frac{R_1}{R_{LSmax}} \right) \quad \therefore R_1 = R_{LSmax} \left(\frac{V_{out1min}}{V_{Ref}} - 1 \right) = 360\ \Omega$$

$$R_{LSmin} = R_1 * \left(\frac{V_{Ref}}{V_{out1max} - V_{Ref}} \right) = 473.7\ \Omega$$

$$R_{DPmin} = 0\text{ k}\Omega \quad R_{DPmax} = 7\text{ k}\Omega$$

$$R_{LSmin} = \frac{R_2 * (R_3 + R_{DPmin})}{R_2 + R_3 + R_{DPmin}} = \frac{R_2 * R_3}{R_2 + R_3} \quad R_{LSmax} = \frac{R_2 * (R_3 + R_{DPmax})}{R_2 + R_3 + R_{DPmax}}$$

Assume $R_3 = 500\ \Omega$,


$$R_2 = \frac{R_{LSmax} * (R_3 + R_{DPmax})}{(R_3 + R_{DPmax}) - R_{LSmax}} = 5\text{ k}\Omega$$

Verify:

$$R_{LSmin} = \frac{R_2 * R_3}{R_2 + R_3} = 455\ \Omega \quad \therefore V_{out2max} = V_{Ref} \left(1 + \frac{R_1}{R_{LSmin}} \right) = 2.24V$$

Notes:

 - V_{Ref} is from the adjustable dual LDO (MIC2211) datasheet
- R_{LSmax} is set to ensure loop stability, not sure of the basis of this value



Resistance Calculations

- For $V_{3.3}$,

$$V_{out2min} = 3V \quad V_{out2max} = 3.6V$$

$$R_{LSmax} = 3 \text{ k}\Omega \quad V_{Ref} = 1.25V$$

$$V_{out2min} = V_{Ref} \left(1 + \frac{R_1}{R_{LSmax}} \right) \quad \therefore R_1 = R_{LSmax} \left(\frac{V_{out2min}}{V_{Ref}} - 1 \right) = 4.2 \text{ k}\Omega$$

$$R_{LSmin} = R_1 * \left(\frac{V_{Ref}}{V_{out2max} - V_{Ref}} \right) = 2.2 \text{ k}\Omega$$

$$R_{DPmin} = 0 \text{ k}\Omega \quad R_{DPmax} = 7 \text{ k}\Omega$$

$$R_{LSmin} = \frac{R_2 * (R_3 + R_{DPmin})}{R_2 + R_3 + R_{DPmin}} = \frac{R_2 * R_3}{R_2 + R_3} \quad R_{LSmax} = \frac{R_2 * (R_3 + R_{DPmax})}{R_2 + R_3 + R_{DPmax}}$$

Assume $R_3 = 5 \text{ k}\Omega$,

$$R_2 = \frac{R_{LSmax} * (R_3 + R_{DPmax})}{(R_3 + R_{DPmax}) - R_{LSmax}} = 4 \text{ k}\Omega$$

Verify:

$$R_{LSmin} = \frac{R_2 * R_3}{R_2 + R_3} = 2.2 \text{ k}\Omega \quad \therefore V_{out2max} = V_{Ref} \left(1 + \frac{R_1}{R_{LSmin}} \right) = 3.64V$$

Notes:

- V_{Ref} is from the dual LDO (MIC2211) datasheet
- R_{LSmax} is set to ensure loop stability in the TI note, not sure of the basis of this value

Resistance Calculations

- For nominal supplies:

$$V_{out1} = 1.8V \quad V_{out2} = 3.3V$$

$$R_{LS} = R_1 * \left(\frac{V_{Ref}}{V_{out} - V_{Ref}} \right)$$

$$\therefore R_{LS1} = 818.2 \, \Omega$$

$$\therefore R_{LS2} = 2.6 \, k\Omega$$

$$R_{LS} = \frac{R_2 * (R_3 + R_{DP})}{R_2 + R_3 + R_{DP}} \quad \therefore R_{DP} = \frac{R_{LS} * (R_2 + R_3) - R_2 R_3}{R_2 - R_{LS}}$$

$$\therefore R_{DP1} = 478 \, \Omega$$

$$\therefore R_{DP2} = 2.4 \, k\Omega$$

$$R_{DP} = \frac{R_{TOT} N}{256} + R_W \quad \therefore N = (R_{DP} - R_W) * \frac{256}{R_{TOT}}$$

$$R_W = 75 \, \Omega$$

$$R_{TOT} = 10 \, k\Omega$$

$$\therefore N_1 = 10.3 \approx 11 \, (Bh)$$

$$\therefore N_2 = 59.5 \approx 60 \, (3Ch)$$

Resistors Components

Output	Resistor	Computed Value	Size 0805 1%
V_{out1}	R_{11}	360 Ω	360 Ω
	R_{12}	5 k Ω	4.99 k Ω
	R_{13}	500 Ω	499 Ω
V_{out2}	R_{21}	4.2 k Ω	4.22 k Ω
	R_{22}	4 k Ω	4.02 k Ω
	R_{23}	5 k Ω	4.99 k Ω

Notes:

- MIC2211 datasheet recommends that to prevent low quiescent current performance being compromised Resistor values are between 100k Ω and 500k Ω . This can't be achieved with the R_{LSmax} assumption

Caravel BB Nucleo Schematic

Notes:

- *MCO* clock is 8 *MHz* on *PF0* and a timer should be used to supply the clock to caravel. I followed [this](#) and I connected the clock to *TIM3_CH2* on *PB5* but I am not sure if this is the right way to do that
- Caravel SPI connected to SPI4 (*PE2 PE4:PE6*) and HKSPI to SPI5 (*PF6:PF9*)
- Caravel UART connected to UART3 (*PC10:PC11*)
- Caravel Reset with \overline{RST}
- Caravel remaining 32 I/Os connected to pins that have no conflict on them and in the WCSP package order
- What should *gpio* connect to?
- Supplies should connect to PWM?
- I connected the supplies to external pin header with *gpio* and *xclk*